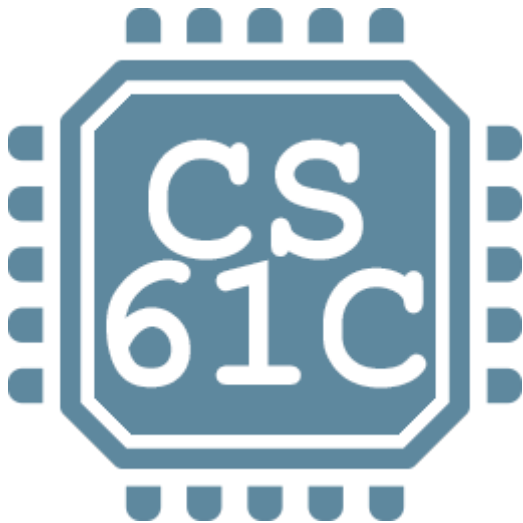


## Q1 Data Multiplexors

3 Points

You can find the lecture slides for todays lecture here!

You can access the YouTube playlist here!



### Q1.1 Which of the following are true?

3 Points

The MUX is most similar to:

- ☐ Variable assignment
- ☐ The `while` loop
- ☒ The `if` statement

---

If I wish to select between  $n$  different inputs to a mux, how many selector bits will I need?


- ☐  $n$
  - ☐  $2^n$
  - ☒  $\log_2(n)$
-

If the boolean expression for a 2-to-1 MUX is  $\bar{s}a + sb$ , then what should the boolean expression for a 4-to-1 MUX be? (Let  $a, b, c, d, s_0, s_1$  be the 4 inputs and 2 selector bits, respectively)

- ☐  $s_1s_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + \bar{s}_1\bar{s}_0d$
- ☐  $s_1s_0a + s_1\bar{s}_0b + \bar{s}_1s_0c + \bar{s}_1\bar{s}_0d$
- ☒  $\bar{s}_1\bar{s}_0a + \bar{s}_1s_0b + s_1\bar{s}_0c + s_1s_0d$
- ☐  $\bar{s}_1\bar{s}_0a + s_1\bar{s}_0b + \bar{s}_1s_0c + s_1s_0d$


## Q2 ALU

4 Points

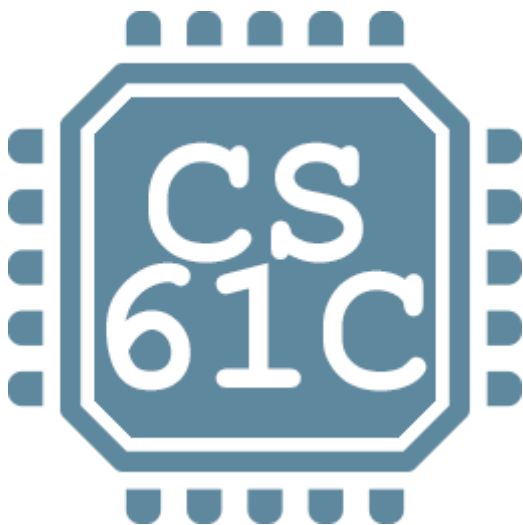

### Q2.1 Which of the following are true?

4 Points

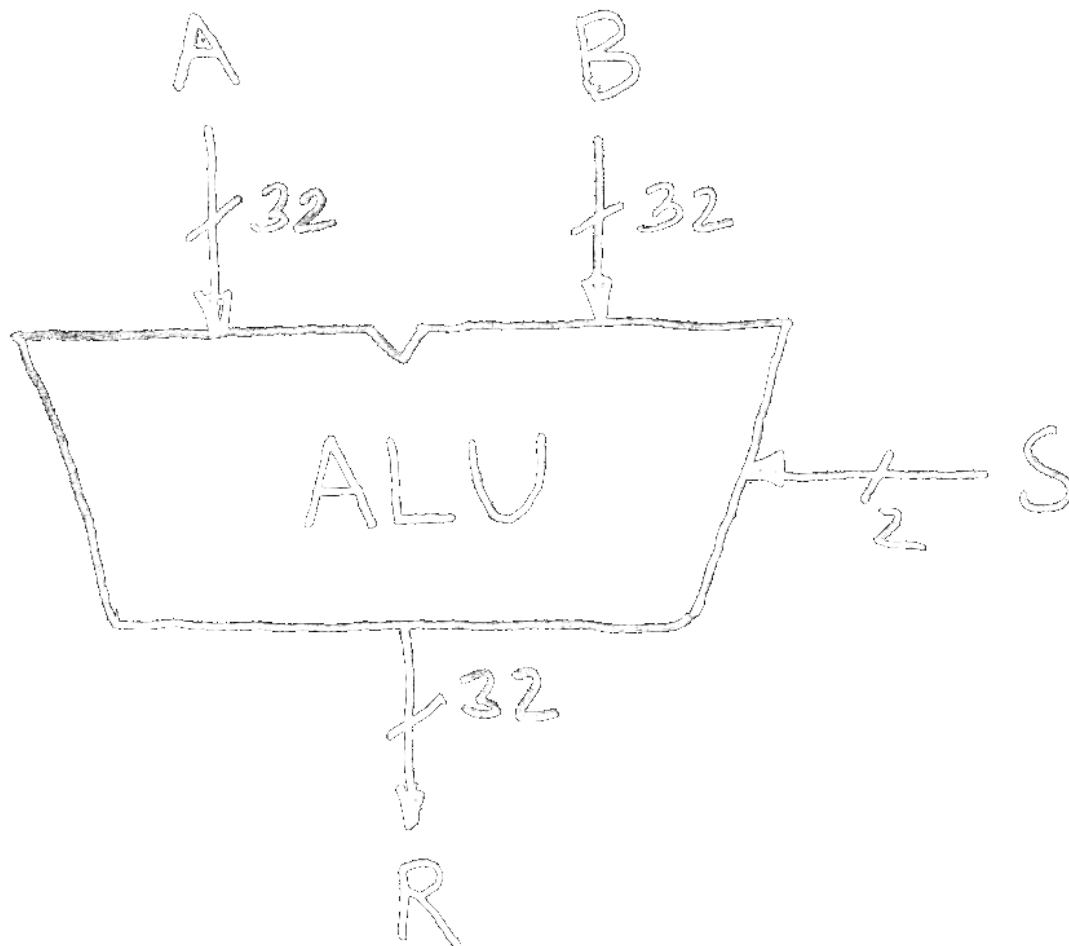

Our ALU will only be able to compute 2 different things, since S is only 2 bits

- ☐ True
- ☒ False

The signal bits S control which operation our ALU does. The machinery for our hardware for the operations not selected are not active.

- ☐ True
- ☒ False

We're going to try to build an adder/subtractor box and reuse machinery (rather than build a separate adder and separate subtractor)

- ☒ True
- ☐ False

We're going to try to build an ANDer/ORer box and reuse machinery (rather than build a separate ANDer and separate ORer)

- ☐ True
- ☒ False

### Q3 Adder/Subtractor

2 Points




#### Q3.1 How do we calculate the overflow of two signed numbers?

2 Points

- ☐ We OR together the  $c_n$  and  $c_{n-1}$  bits
- ☐ We AND together the  $c_n$  and  $c_{n-1}$  bits
- ☒ We XOR together the  $c_n$  and  $c_{n-1}$  bits
- ☐ We XNOR together the  $c_n$  and  $c_{n-1}$  bits

### Q4 Subtractor Design

4 Points

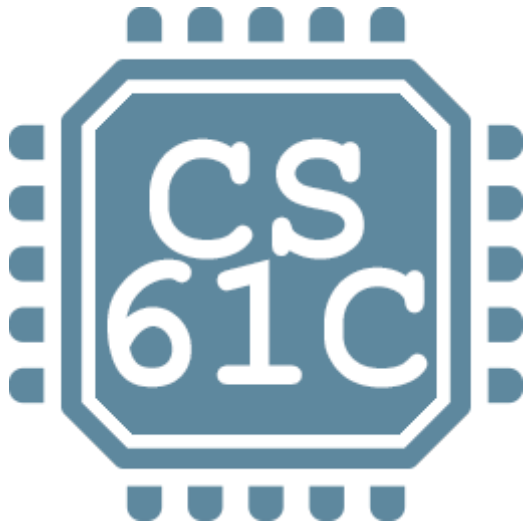

**Q4.1** Which of the following are true?

4 Points

How did we implement subtraction?

- ☐ We built a whole new subtraction unit
- ☒ We leveraged the 2's complement trick of negating a number by flipping the bits and adding 1
- ☐ We leveraged the 2's complement trick of negating a number by flipping the bits
- ☒ We leveraged the mathematical fact that  $a - b == a + (-b)$
- ☐ We flipped one input's bits by ANDing them all with 1
- ☐ We flipped one input's bits by ANDing them all with 0
- ☐ We flipped one input's bits by ORing them all with 1
- ☒ We flipped one input's bits by XORing them all with 1
- ☐ We flipped one input's bits by XORing them all with 0
- ☐ We added 1 to one input by adding one more addition unit that will manually add a constant 1
- ☒ We added 1 to one input by inserting a carry-in bit  $c_0$
- ☒ We connected the flipping bit and the +1 together

## Lecture 17 - Combinational Logic Blocks

● UNGRADED

STUDENT

Shauna Hannani

**TOTAL POINTS**

**- / 13 pts**

**QUESTION 1**

Data Multiplexors

3 pts

1.1 Which of the following are true?

3 pts

**QUESTION 2**

ALU

4 pts

2.1 Which of the following are true?

4 pts

**QUESTION 3**

Adder/Subtractor

2 pts

3.1 How do we calculate the overflow of two signed numbers?

2 pts

**QUESTION 4**

Subtractor Design

4 pts

4.1 Which of the following are true?

4 pts